



4-Bit Arithmetic Logic Unit (ALU) by CMOS.

Team:

Adham Ahmed Hammada — 18100846

Ahmed Mohamed Fouad — 18101467

Under the Supervision of

Dr. Ahmed H.Madian

Eng. Alaa Osama

Submitted for ECEN-302/312 Analysis and Design of Digital Circuits Course Project

Contents

Introduction.....	4
Components of ALU.....	5
Inverter Gate & 4-Inverter Gate.....	5
AND Gate & 4-AND Gate.....	6
OR Gate & 4-OR Gate.....	8
XOR Gate	10
3-1 AND Gate, 4-1 AND Gate, 5-1 AND Gate	11
3-1 OR Gate, 4-1 OR Gate, 5-1 OR Gate	14
2x1 MULTIPLEXER && 4 (2x1) Multiplexer	17
4x1 MULTIPLEXER.....	19
CARRY LOOK AHEAD ADDER	21
P & G Generator (Half Adder):.....	21
Carry Lookahead (CLA):	22
Adder:	22
RIPPLE ADDER	25
Assembly	27
ALU by carry lookahead adder.....	27
ALU by ripple adder	28
Testing	29
And Testing.....	30
A B Testing	31
A + B Testing.....	32
Not Used	33
A & ~B.....	34
A ~B	35
A - B.....	36
SLT	37
Results.....	38
Propagation delay.....	38
ALU with carry lookahead adder:.....	38
ALU with ripple adder	38
Maximum power consumption	39

ALU by carry lookahead adder.....	39
ALU by ripple adder	40
Comparison and conclusion	41

Figures


Figure 1 Functions of the ALU	4
Figure 2 Inverter Symbol.....	5
Figure 3 Inverter Circuit	5
Figure 4 4-inverter symbol.....	5
Figure 5 Four-inverter circuit	5
Figure 6 A gate circuit	6
Figure 7 AND gate symbol.....	6
Figure 8 Four-AND gate symbol.....	7
Figure 9 Four AND gate circuit.....	7
Figure 10 OR Circuit	8
Figure 11 OR Gate symbol	8
Figure 12 Four-OR Symbol	9
Figure 13 Four-OR circuit	9
Figure 14 XOR Circuit	10
Figure 15 XOR Symbol.....	10
Figure 16 3-1 AND circuit	11
Figure 17 4-AND symbol	11
Figure 18 4-AND circuit.....	12
Figure 19 4-AND symbol	12
Figure 20 5-1 AND gate circuit	13
Figure 21 5-1 AND symbol	13
Figure 22 3-1 OR Circuit	14
Figure 23 3-1 OR gate symbol	14
Figure 24 4-1 OR Gate circuit.....	15
Figure 25 4-1 OR symbol.....	15
Figure 26 5-1 OR circuit.....	16
Figure 27 5-1 OR gate.....	16
Figure 28 2x1 Multiplexer Circuit.....	17
Figure 29 2x1 Multiplexer symbol.....	17
Figure 30 4 2x1 Multiplexer circuit	18
Figure 31 4 2x1 Multiplexer symbol.....	18
Figure 32 4x1 Multiplexer symbol.....	19
Figure 33 4x1 Multiplexer Circuit.....	19
Figure 34 4 4x1 Multiplexer symbol.....	20

Figure 35 4 4x1 Multiplexer circuit	20
Figure 36 P & G generator circuit.....	21
Figure 37 Carry Look Ahead Circuit.....	22
Figure 38 Adder circuit.....	23
Figure 39 Full circuit of CLA ADDER	24
Figure 40 Full adder circuit	25
Figure 41 Full adder symbol.....	26
Figure 42 4 Full adders connected (Ripple adder)	26
Figure 43 Full ALU circuit with CLA	27
Figure 44 Full ALU circuit with ripple adder.....	28
Figure 45 Results of the functions graph	29
Figure 46 A & B.....	30
Figure 47 A B	31
Figure 48 A + B	32
Figure 49 Not Used	33
Figure 50 A & ~B.....	34
Figure 51 A ~B	35
Figure 52 A - B	36
Figure 53 SLT test.....	37
Figure 54 CLA Propagation delay	38
Figure 55 Ripple Adder propagation delay	38
Figure 56 ALU with CLA Power Consumption	39
Figure 57 ALU with ripple adder power consumption.....	40

Introduction

In this report we will implement a 4-bit Arithmetic Logic Unit (ALU) using two different types of adders: The Ripple Carry Adder and Carry Lookahead Adder. Furthermore, the performance of the two ALUs, regarding the number of transistors, worst-case propagation delay, and maximum power consumption, must be evaluated and summarized in a table of comparison. The ALUs will be designed using CMOS logic with the following specifications:

 - 1) The supply voltage is 1.2V.
- 2) Use the minimum channel length that is allowed by the technology file.
- 3) The rise time and fall time of the ALU's inputs are 100ps each.
- 4) Each logic gate must have symmetric propagation delays (TPHL=TP LH) under the worst-case scenarios. The propagation delay is the time between the point at which the input changes by 50% and the point at which the output changes by 50%.
- 5) The load capacitance of each output pin, Y(3:0), is 1pF.



$F_{2:0}$	Function
000	$A \& B$
001	$A B$
010	$A + B$
011	not used
100	$A \& \sim B$
101	$A \sim B$
110	$A - B$
111	SLT

Figure 1 Functions of the ALU

Components of ALU

Inverter Gate & 4-Inverter Gate

The inverter gate was implemented as follows (one PMOS along with one NMOS)

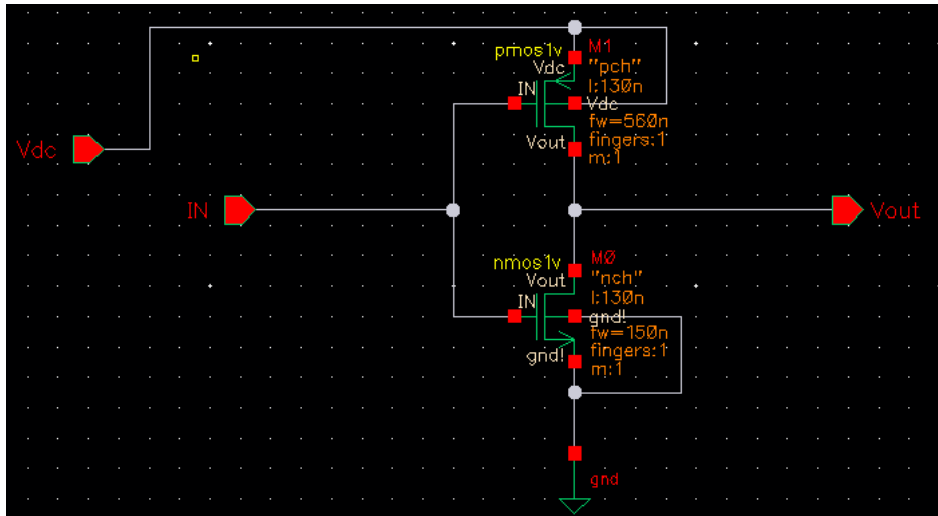


Figure 3 Inverter Circuit

 


Figure 2 Inverter Symbol

Then to make a 4-bit inverter we combined 4 inverters together.

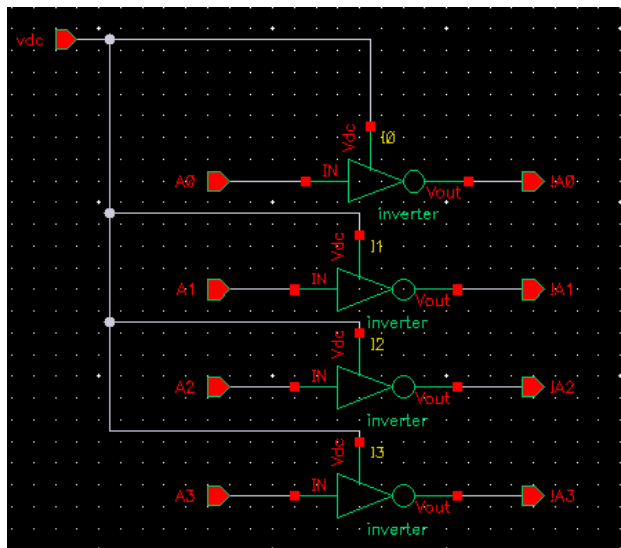


Figure 5 Four-inverter circuit

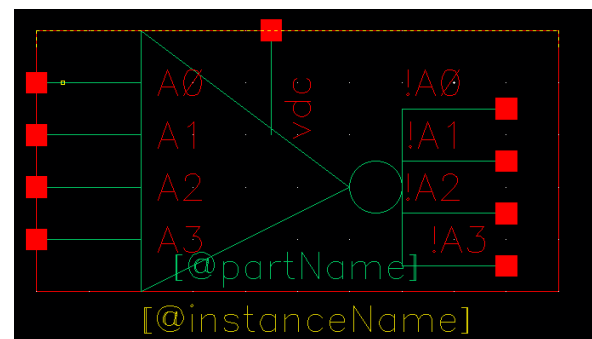


Figure 4 4-inverter symbol

We adjusted the sizing of the inverter to be $w = 560n$ for PMOS and $w = 150n$ for NMOS.

AND Gate & 4-AND Gate

The AND gate was implemented as follows (two parallel PMOS along with two series NMOS).

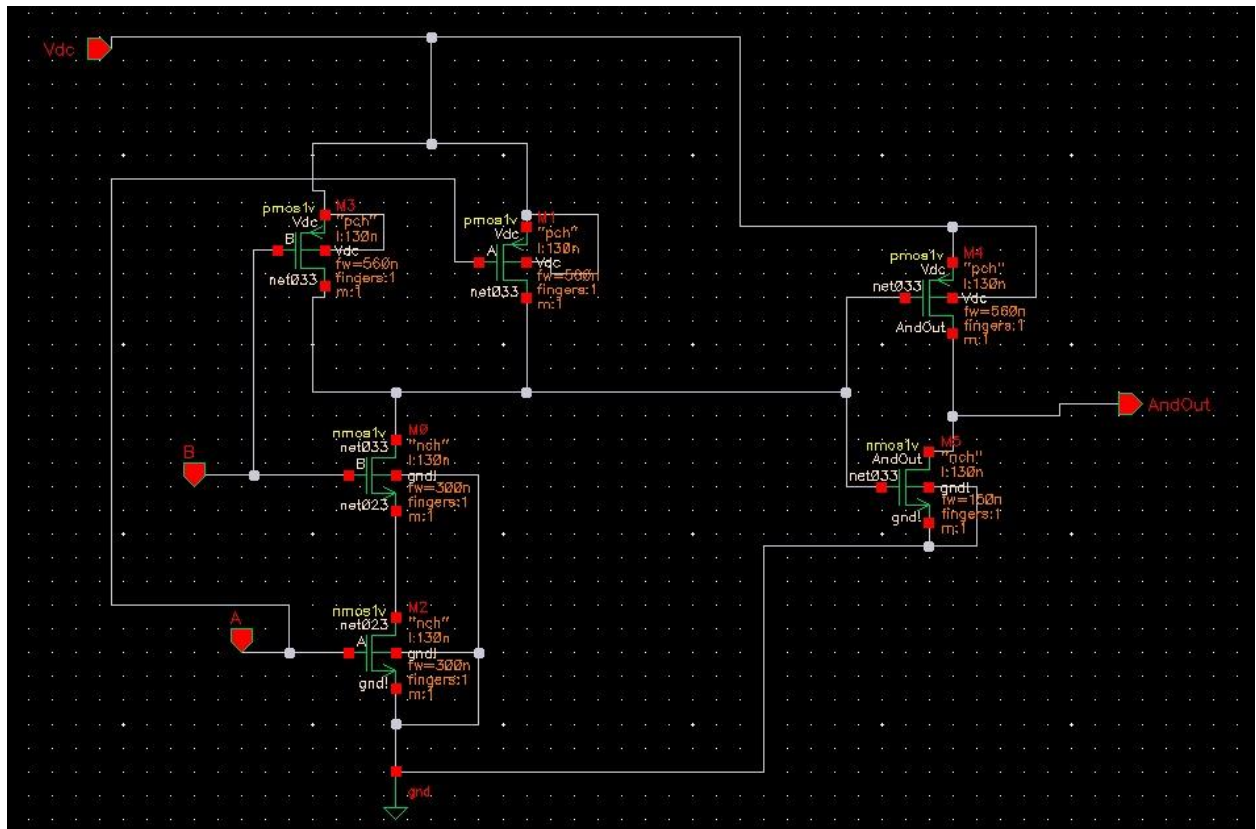


Figure 6 A gate circuit

 


Figure 7 AND gate symbol

Then to design a 4-bit AND we combined 4 AND gates

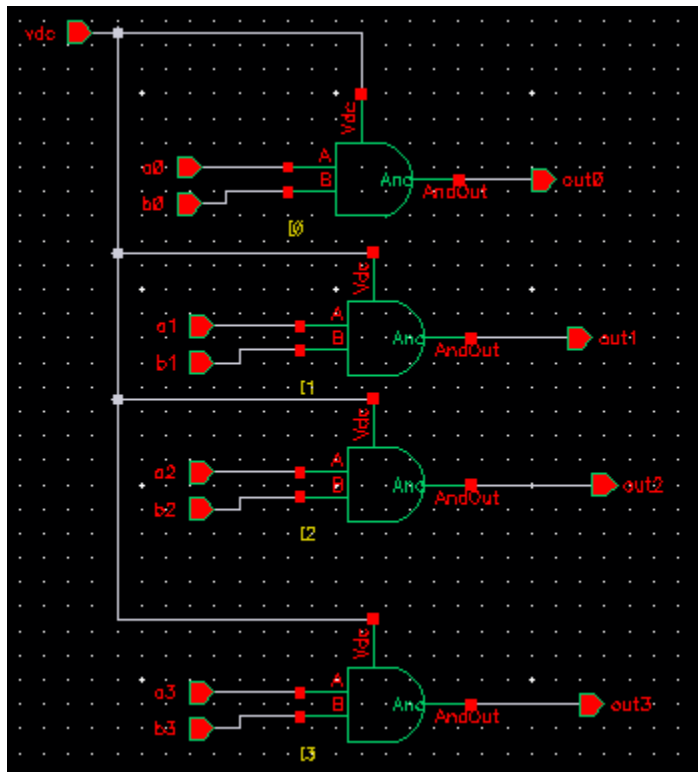


Figure 9 Four AND gate circuit

We adjusted the sizing of the AND gate to be $w=560n$ for PMOS and $w=300n$ for NMOS.

 


Figure 8 Four-AND gate symbol

OR Gate & 4-OR Gate

The OR gate was implemented as follows (two series PMOS along with two parallel NMOS)

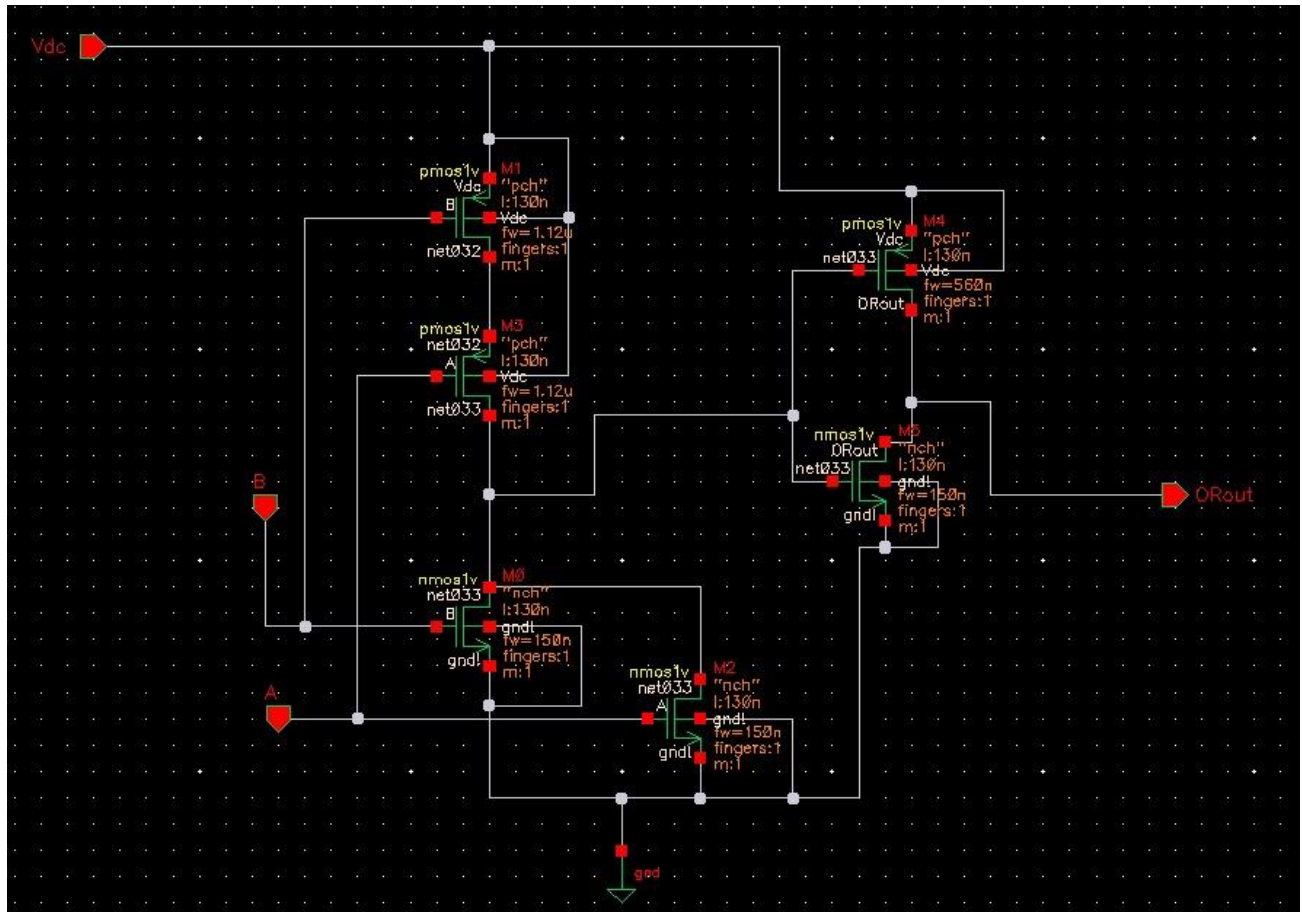


Figure 10 OR Circuit

 


Figure 11 OR Gate symbol

Then to design a 4-bit OR we combined 4 OR gates

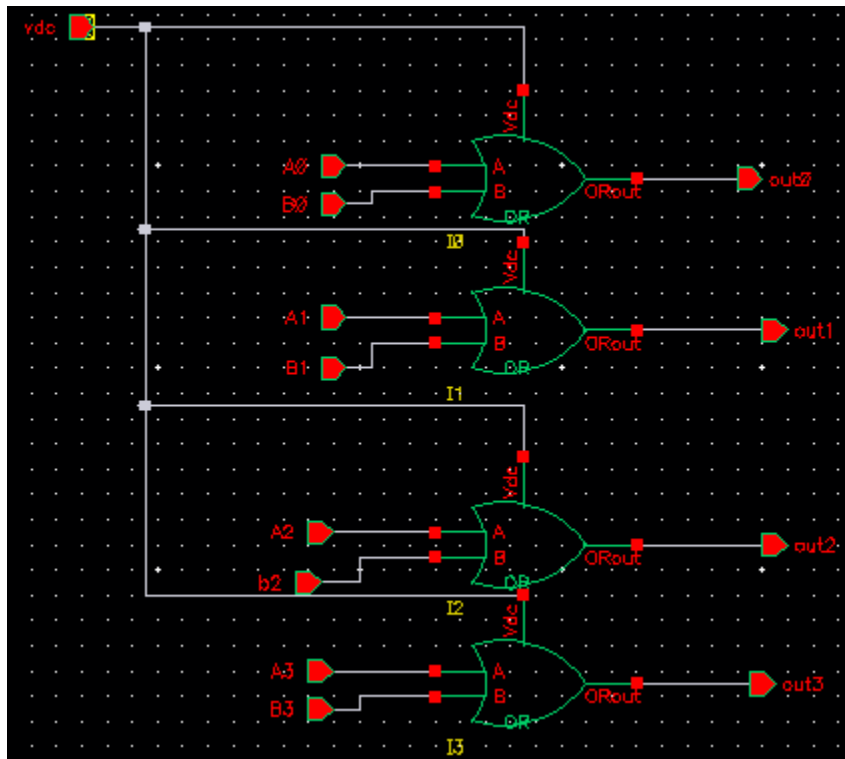


Figure 13 Four-OR circuit

We adjusted the sizing of the gate to be $w=1120n$ for PMOS and $w=150n$ for NMOS.

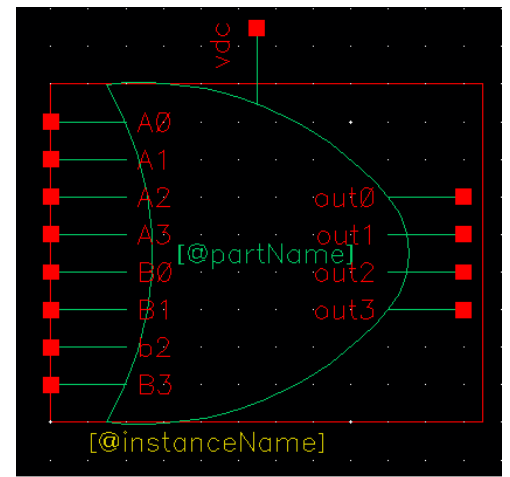


Figure 12 Four-OR Symbol

XOR Gate

The XOR Gate was implemented using two Inverter gates, two AND gates and one OR gate as shown below.

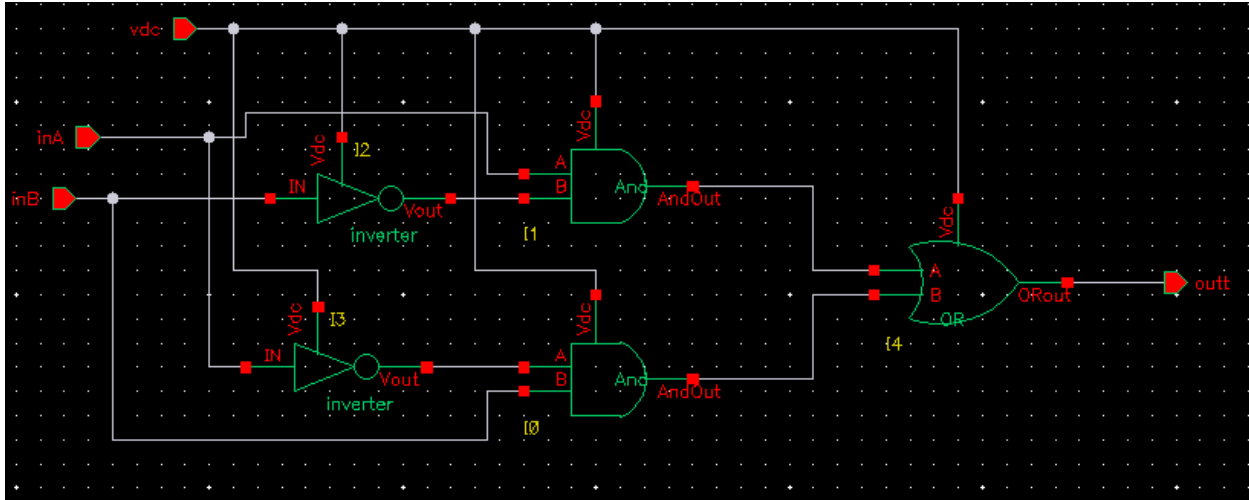


Figure 14 XOR Circuit

 


Figure 15 XOR Symbol

3-1 AND Gate, 4-1 AND Gate, 5-1 AND Gate

The 3-1 AND gate was designed as shown below (three parallel PMOS along with three series NMOS)

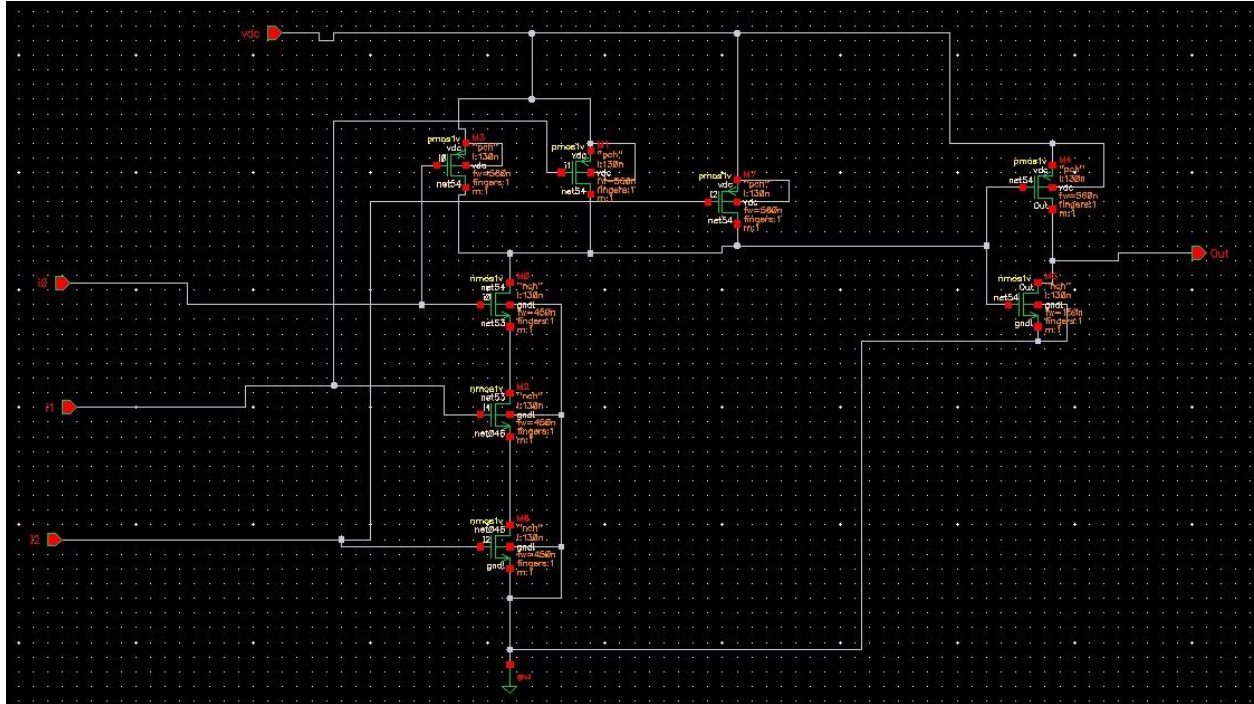


Figure 16 3-1 AND circuit

We adjusted the sizing of the gate to be
w=450n for NMOS and w=560n for PMOS

 


Figure 17 4-AND symbol

The 4-1 AND gate was designed as shown below (four parallel PMOS along with four series NMOS)

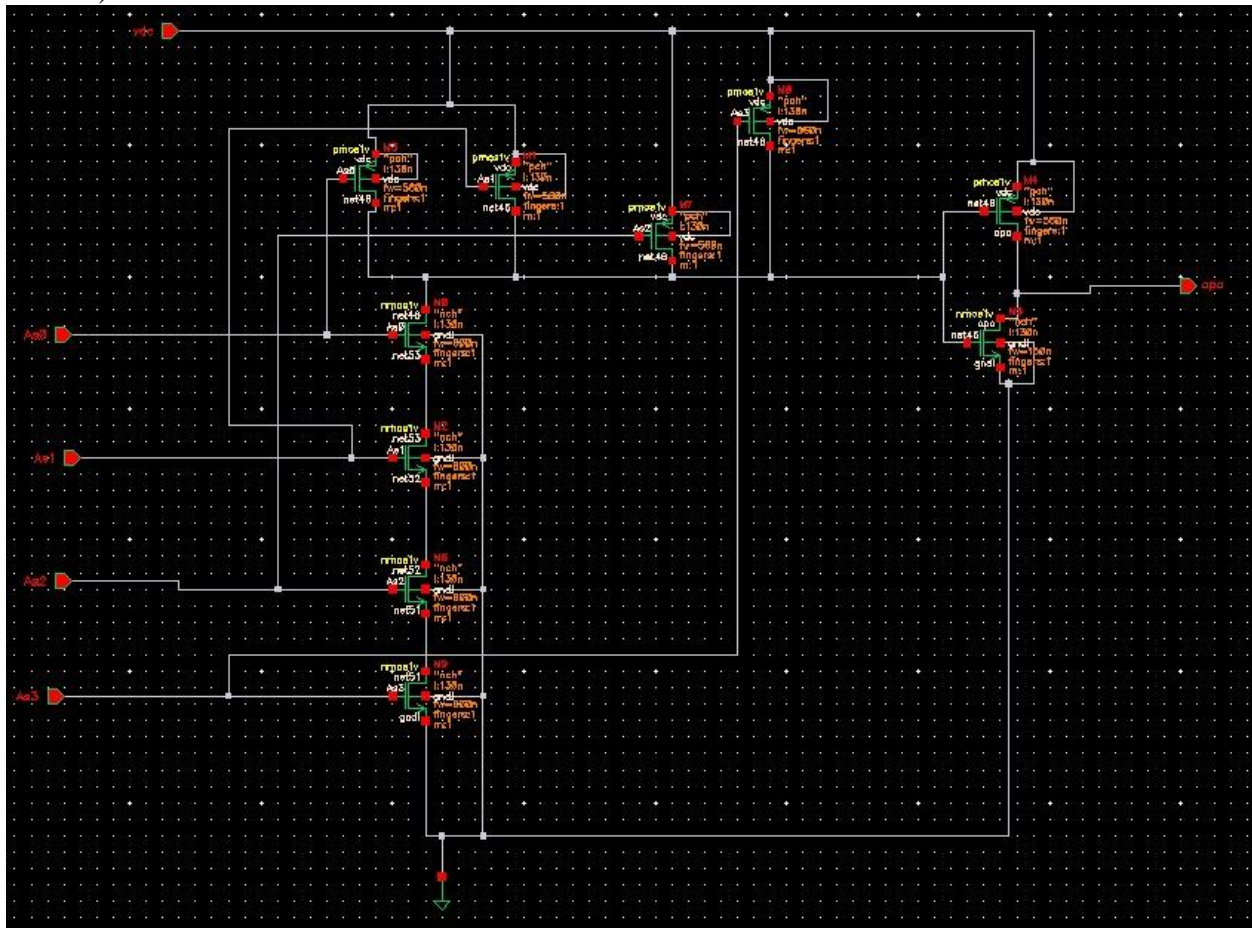


Figure 18 4-AND circuit

We adjusted the sizing of the gate to be
w=600n for NMOS and w=560n for PMOS

 


Figure 19 4-AND symbol

The 5-1 AND gate was designed as shown below (five parallel PMOS along with five series NMOS)

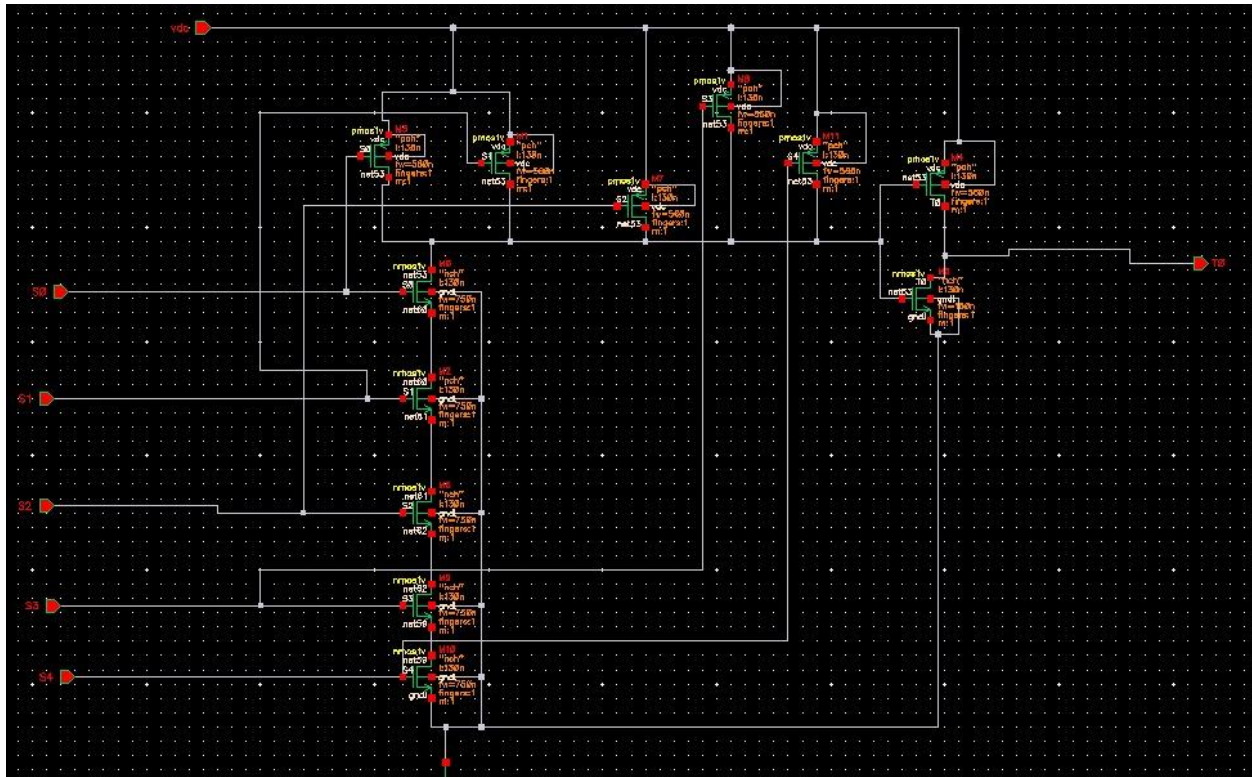


Figure 20 5-1 AND gate circuit

We adjusted the sizing of the gate to be $w=750n$ for NMOS and $w=560n$ for PMOS

 


Figure 21 5-1 AND symbol

3-1 OR Gate, 4-1 OR Gate, 5-1 OR Gate

The 3-1 OR gate was implemented as follows (three series PMOS along with three parallel NMOS)

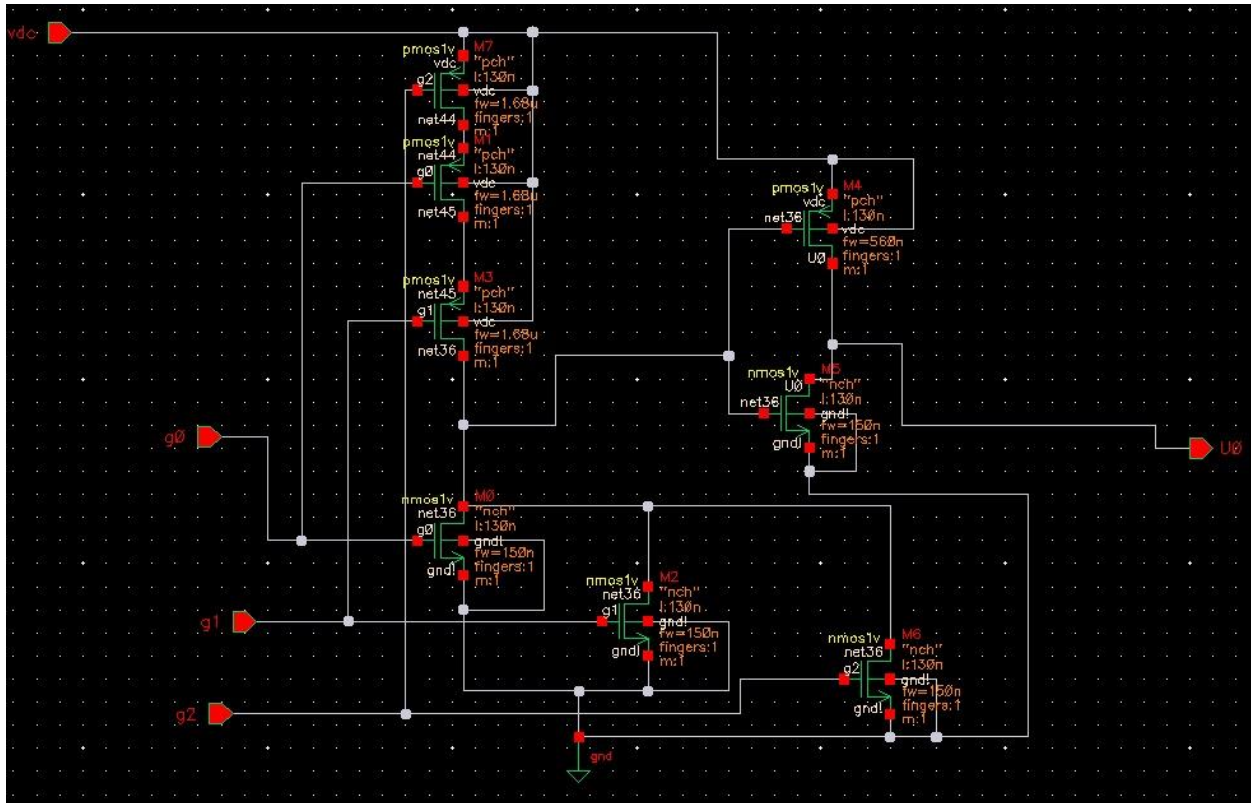


Figure 22 3-1 OR Circuit

We adjusted the sizing of the gate to be
w=150n for NMOS and w=1680n for PMOS

 


Figure 23 3-1 OR gate symbol

The 4-1 OR gate was implemented as follows (four series PMOS along with four parallel NMOS)

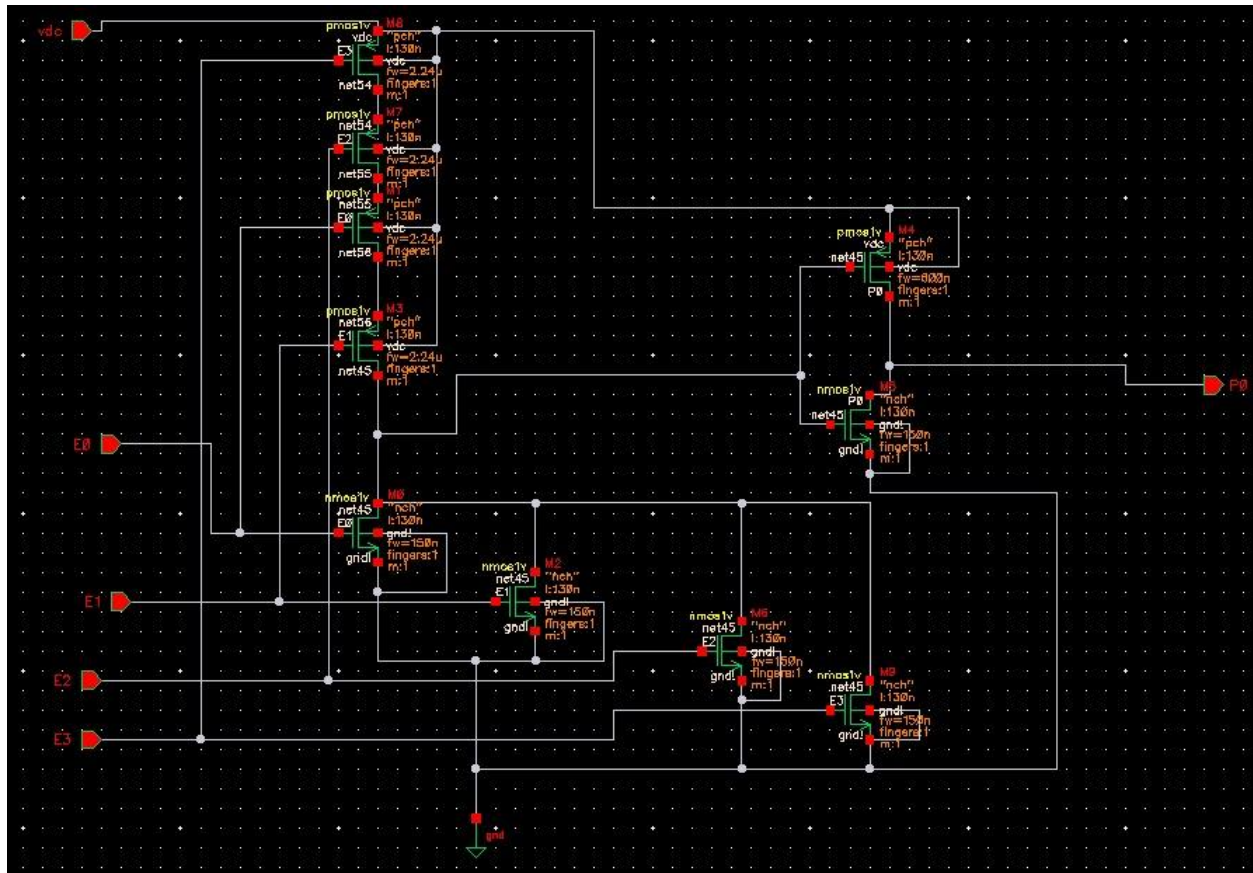


Figure 24 4-1 OR Gate circuit

We adjusted the sizing of the gate to be
w=150n for NMOS and w=2240n for PMOS

 


Figure 25 4-1 OR symbol

The 5-1 OR gate was implemented as follows (five series PMOS along with five parallel NMOS)

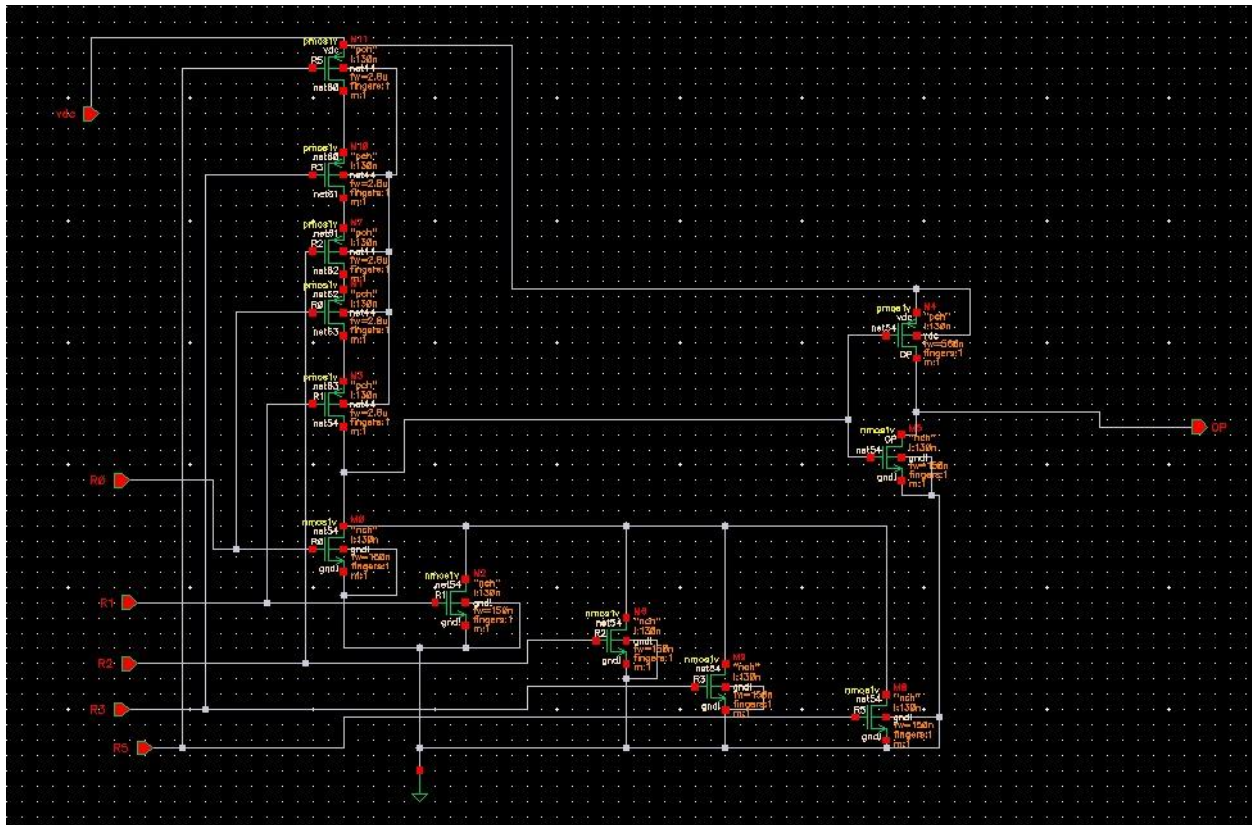


Figure 26 5-1 OR circuit

We adjusted the sizing of the gate to be $w=150n$ for NMOS and $w=2800n$ for PMOS

 


Figure 27 5-1 OR gate

2x1 MULTIPLEXER & 4 (2x1) Multiplexer

The 2x1 Multiplexer is implemented as follows (One inverter gate, two AND gates, and one OR gate)

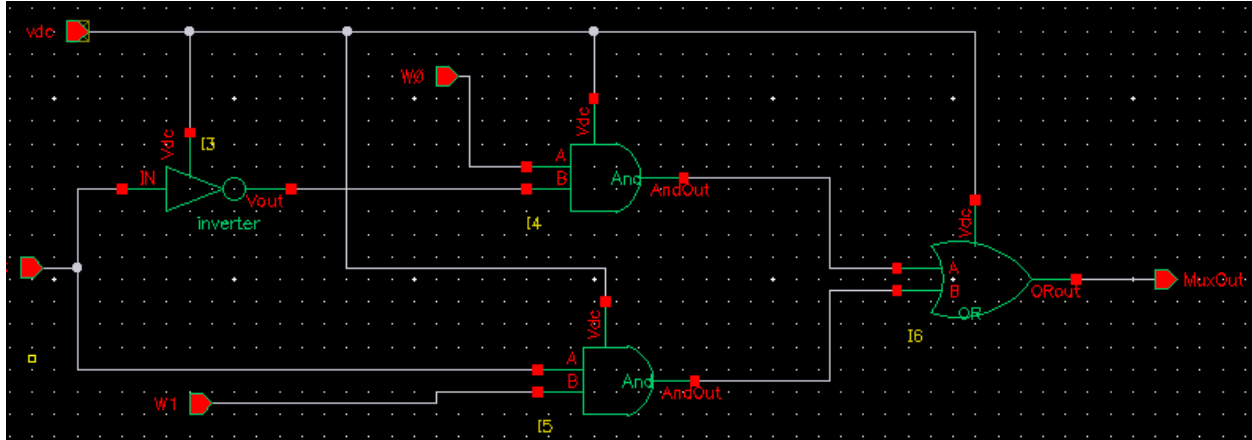


Figure 28 2x1 Multiplexer Circuit

 


Figure 29 2x1 Multiplexer symbol

The 4 (2x1) Multiplexer was implemented using 4 2x1 Multiplexers.

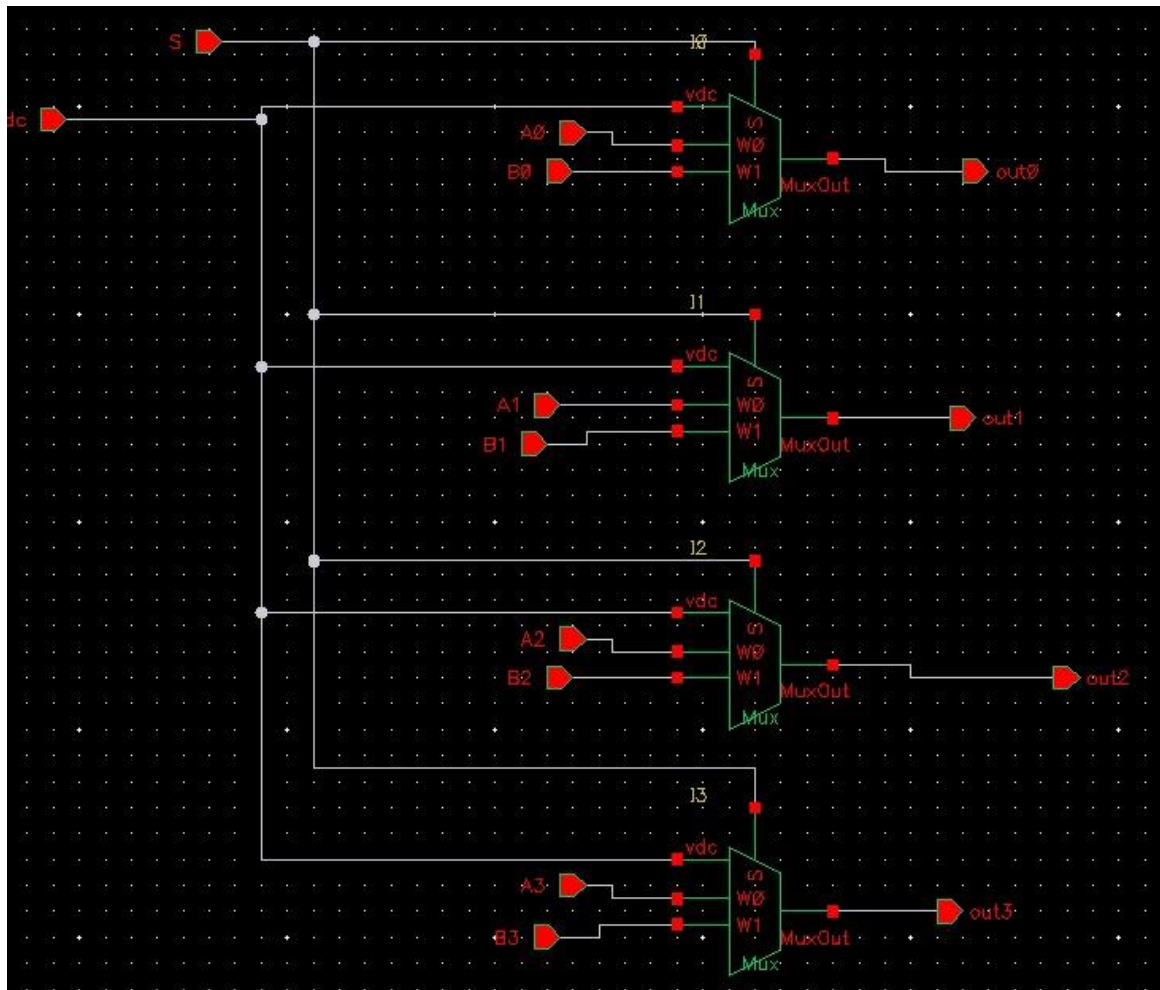


Figure 30 4 2x1 Multiplexer circuit

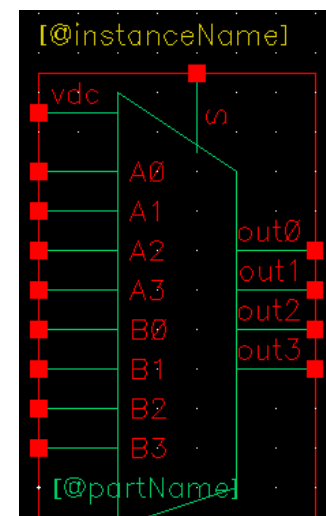


Figure 31 4 2x1 Multiplexer symbol

4x1 MULTIPLEXER

The 4x1 Multiplexer was implemented using two inverter gates, four 3-1 AND gates, one 4-1 OR gate

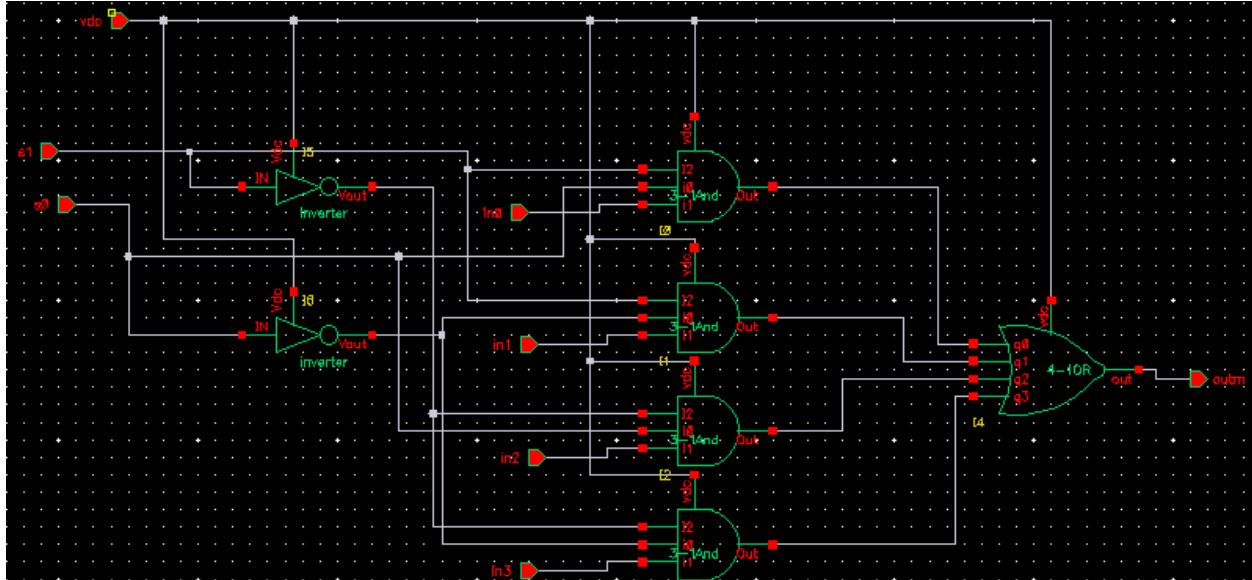


Figure 33 4x1 Multiplexer Circuit

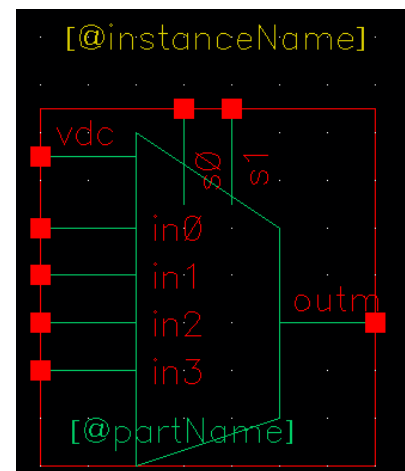


Figure 32 4x1 Multiplexer symbol

The 4 (4x1) Multiplexer was implemented using 4 4x1 Multiplexers.

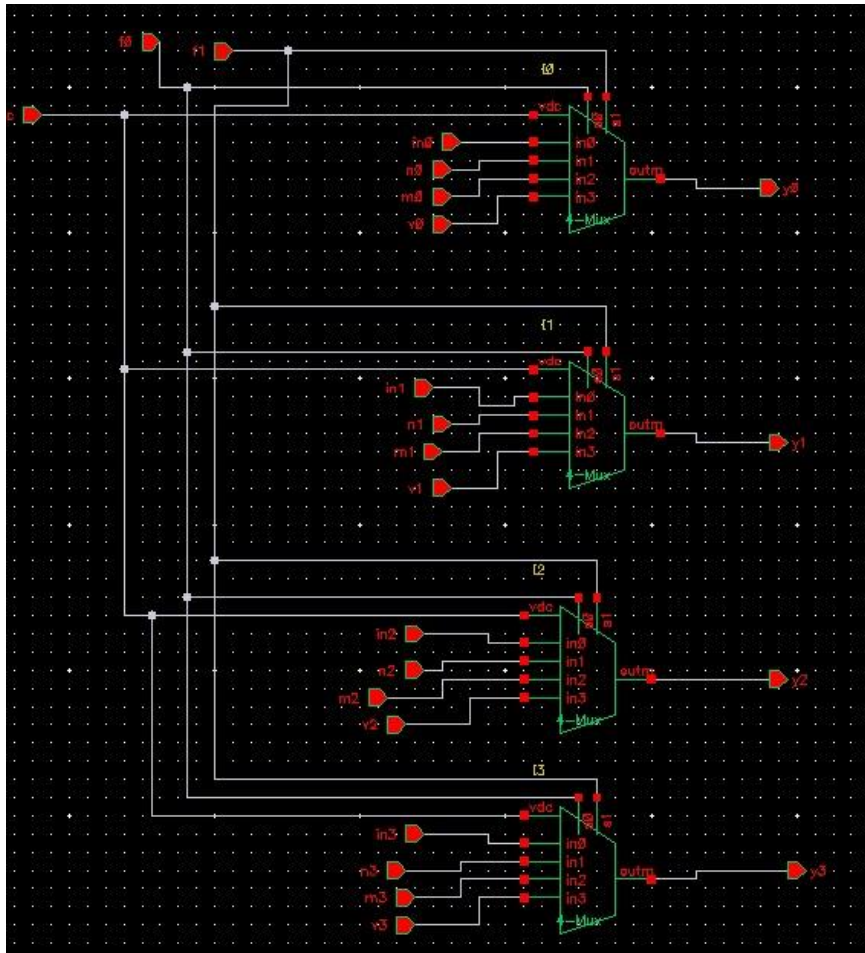


Figure 35 4 4x1 Multiplexer circuit

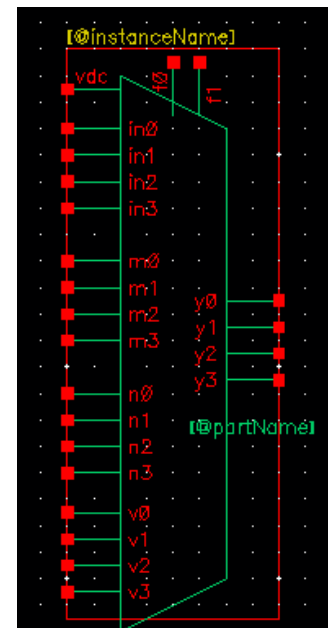


Figure 34 4x1 Multiplexer symbol

CARRY LOOK AHEAD ADDER

The carry look ahead ADDER consists of three parts: P & G generator, Carry look ahead, and Adder.

P & G Generator (Half Adder):

This block consists of half adders used for generating P and G terms of each bit and generate these terms needed for the CLA because the carry depends on it.

$$\text{Carry} = AB + \text{Cin} (A \text{ XOR } B)$$

Where (A XOR B) is called carry propagate (known as P) because it propagates the Cin from previous stage to the next stage. And AB is called carry generate (known as G) because it can directly generate carry bit without any Cin.

P and G terms for a 4-bit number will be:

$$P_0 = (A_0 \text{ XOR } B_0) , G_0 = A_0 B_0$$

$$P_1 = (A_1 \text{ XOR } B_1) , G_1 = A_1 B_1$$

$$P_2 = (A_2 \text{ XOR } B_2) , G_2 = A_2 B_2$$

$$P_3 = (A_3 \text{ XOR } B_3) , G_3 = A_3 B_3$$

The P & G generator circuit is shown below:

 


Figure 36 P & G generator circuit

Carry Lookahead (CLA):

CLA block contains combinational circuit used to determine the carry bits. it takes Augend, Addend and carry in as inputs and produce the carry bits. Consider A, B two numbers being added both 4 bits wide and C_0 as carry in. And C_1, C_2, C_3, C_4 are the output carry bits.

First we will derive C_1, C_2, C_3, C_4 using the carry equation from full adder.

$$\text{Carry} = AB + C_{in} (A \text{ XOR } B)$$

$$P = (A \text{ XOR } B)$$

$$G = AB$$

$$\text{Carry} = G + C_{in}P$$

So C_1, C_2, C_3, C_4 will become:

$$C_1 = G_0 + C_0P_0$$

$$C_2 = G_1 + C_1P_1 = G_1 + (G_0 + C_0P_0)P_1 = G_1 + G_0P_1 + C_0P_0P_1$$

$$C_3 = G_2 + C_2P_2 = G_2 + (G_1 + G_0P_1 + C_0P_0P_1)P_2 = G_2 + G_1P_2 + G_0P_1P_2 + C_0P_0P_1P_2$$

$$C_4 = G_3 + C_3P_3 = G_3 + (G_2 + G_1P_2 + G_0P_1P_2 + C_0P_0P_1P_2)P_3 = G_3 + G_2P_3 + G_1P_2P_3 + G_0P_1P_2P_3 + C_0P_0P_1P_2P_3$$

Thus, it shows that none of these carry bits depend on their previous stage carry bits. They only need A, B and C_0 . This carry look ahead block will generate these carry bits and provide it to the adders block for addition. The circuit of the carry look ahead is shown below:

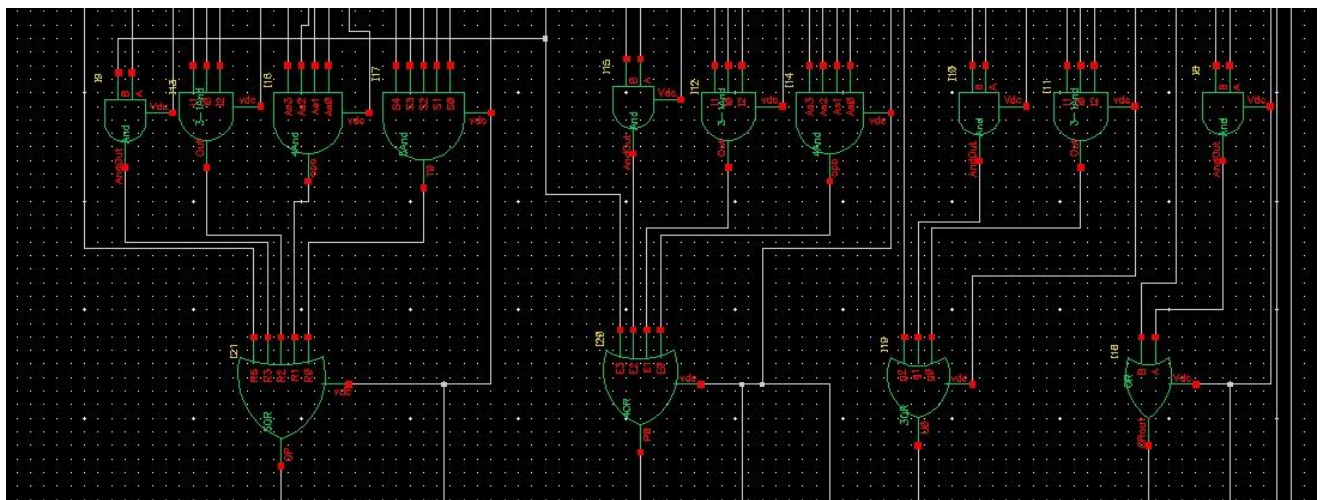


Figure 37 Carry Look Ahead Circuit

Adder:

As we know that the carry bits will be provided by the CLA block, so we don't need Full adders to evaluate the carry bits. We only need the sum which is:

$$S = C_{in} \text{ XOR } (A \text{ XOR } B)$$

So the sum of each bit will be

$$S_0 = C_0 \text{ XOR } (A_0 \text{ XOR } B_0) = C_0 \text{ XOR } (P_0)$$

$$S_1 = C_1 \text{ XOR } (A_1 \text{ XOR } B_1) = C_1 \text{ XOR } (P_1)$$

$$S_2 = C_2 \text{ XOR } (A_2 \text{ XOR } B_2) = C_2 \text{ XOR } (P_2)$$

$$S_3 = C_3 \text{ XOR } (A_3 \text{ XOR } B_3) = C_3 \text{ XOR } (P_3)$$

And the last carry C_4 will be the C_{out} of the **CLA full adder**.

$$C_{out} = C_4$$

The circuit of the Adder is shown below:

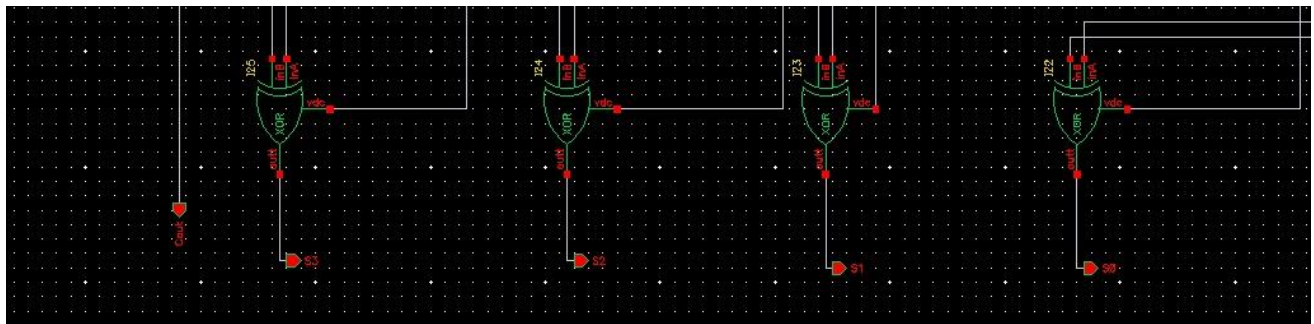


Figure 38 Adder circuit

The full circuit of the CLA adder is shown below:

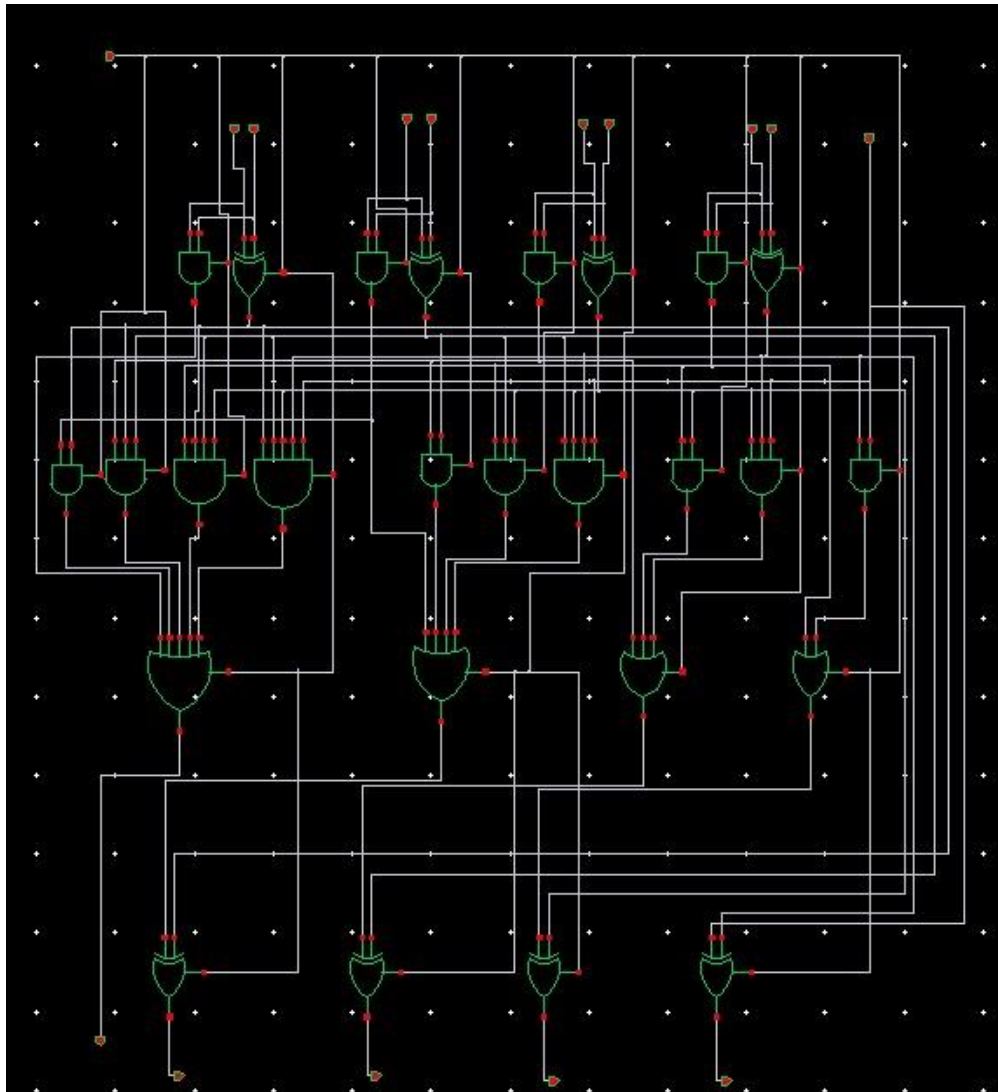


Figure 39 Full circuit of CLA ADDER

RIPPLE ADDER

A Full adder was implemented by the following equations

$$S_i = A_i \oplus B_i \oplus C_i$$

$$C_i = C_{i-1}(A_i \oplus B_i) + A_i B_i$$

The circuit of the full adder is shown below:

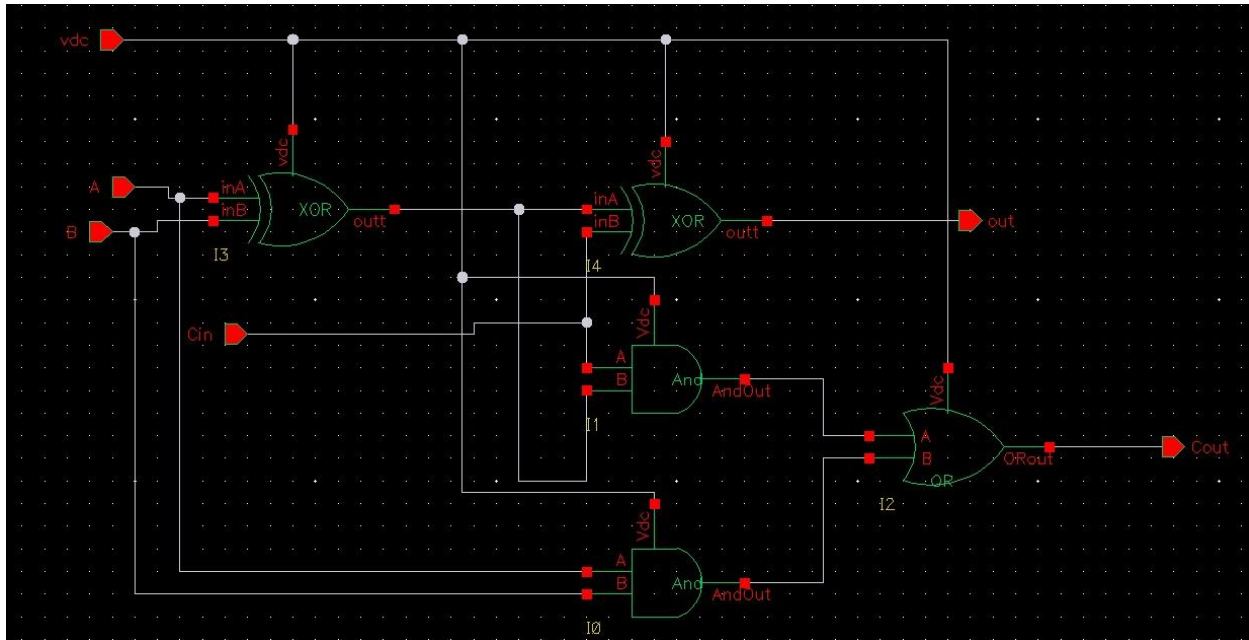


Figure 40 Full adder circuit

Then the Ripple adder was implemented by four full adders as shown below:

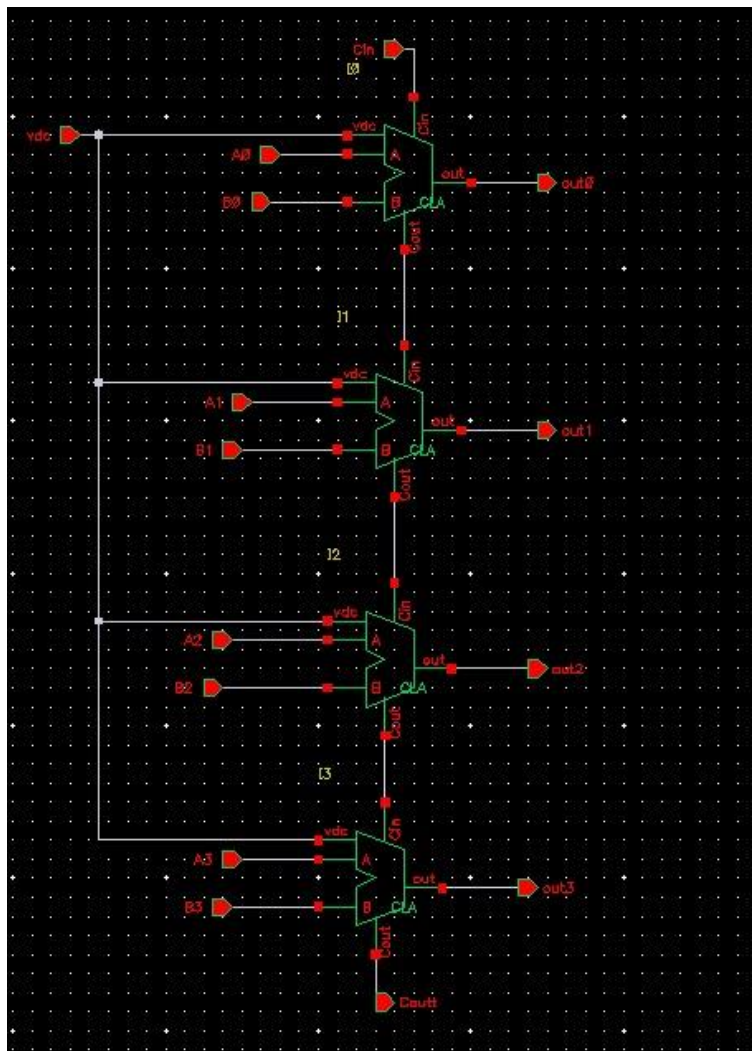


Figure 42 4 Full adders connected (Ripple adder)

 


Figure 41 Full adder symbol

Assembly

ALU by carry lookahead adder

The assembly of the components of the ALU with CLA is shown below.

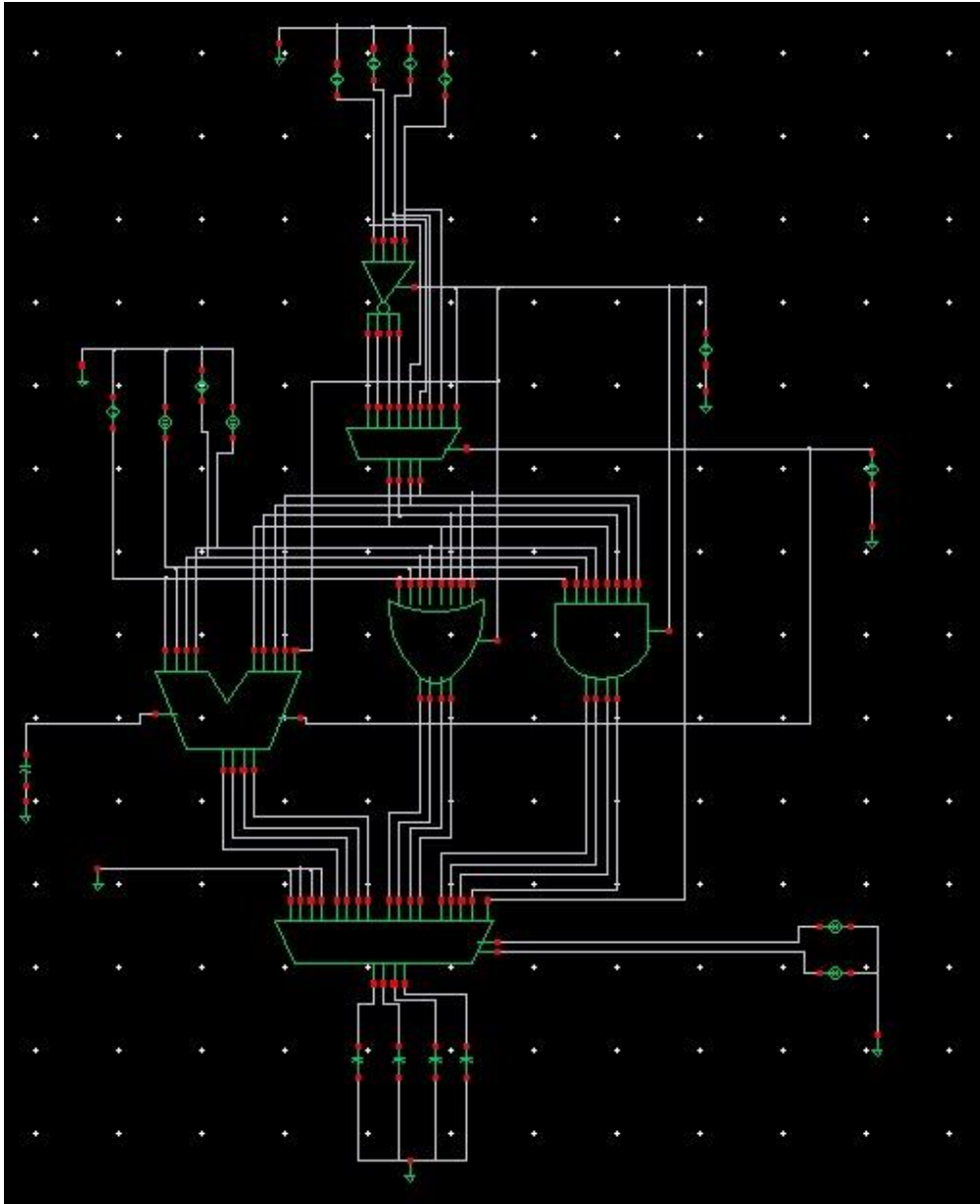


Figure 43 Full ALU circuit with CLA

ALU by ripple adder

The assembly of the components of the ALU with ripple adder is shown below.

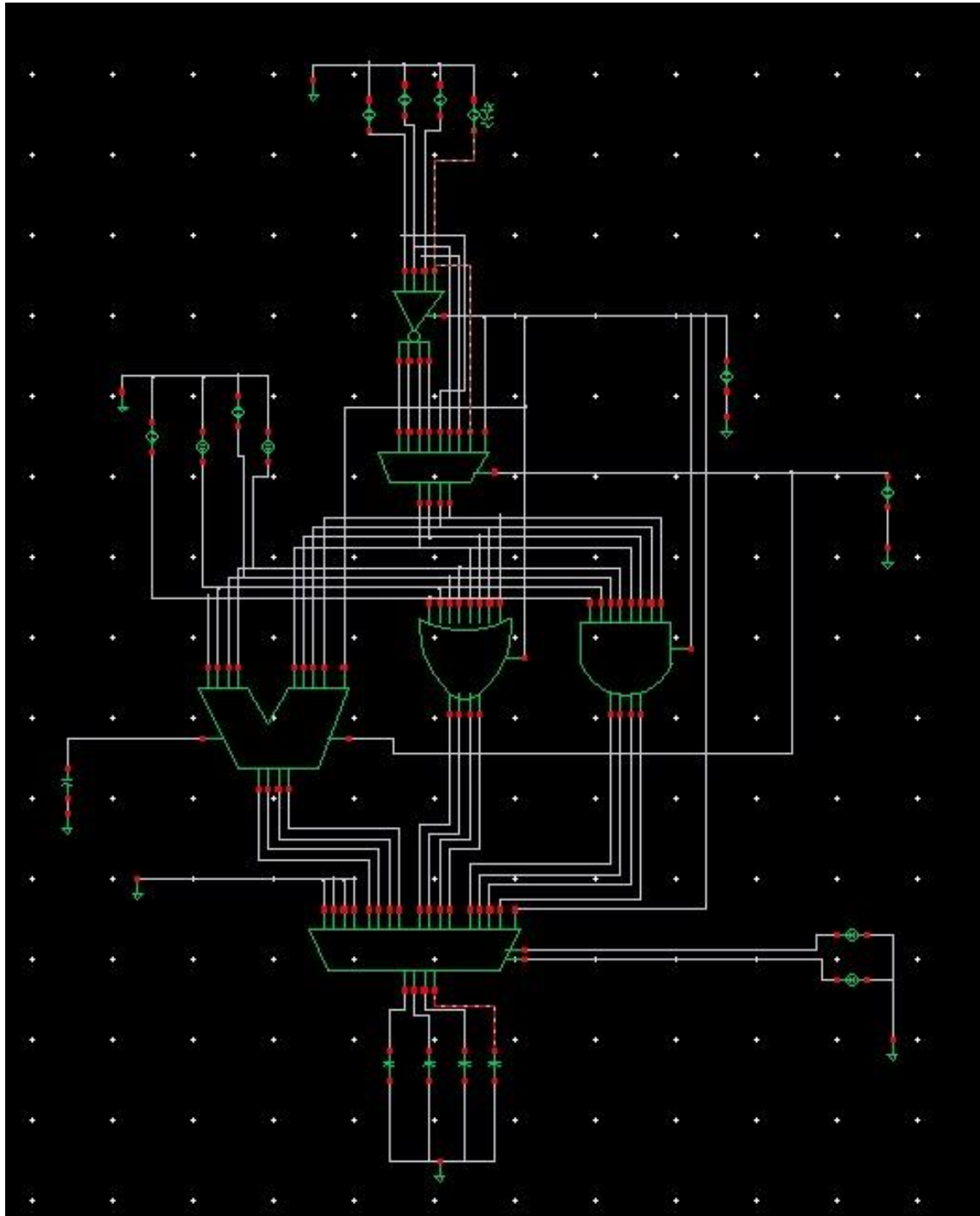


Figure 44 Full ALU circuit with ripple adder

Testing

To test the performance of the ALU circuit we put $A = 0111(7)$, $B = 0101(5)$, the results of the functions is shown in the following table:

F2:0	Function	Result
000	&	0101
001		0111
010	+	1100
011	~used	0000
100	$A \& \sim B$	0010
101	$A \sim B$	1111
110	$A - B$	0010
111	SLT	0001

The following graph shows the results:

 


Figure 45 Results of the functions graph

And Testing

F2:0	Function	Result
000	&	0101

 


Figure 46 A & B

A | B Testing

F2:0	Function	Result
001		0111

The result is shown in the graph below:

 


Figure 47 A | B

A + B Testing

F2:0	Function	Result
010	+	1100

 


Figure 48 A + B

Not Used

F2:0	Function	Result
011	~used	0000

 


Figure 49 Not Used

A & ~B

F2:0	Function	Result
100	A & ~B	0010

 


Figure 50 A & ~B

A | ~B

F2:0	Function	Result
100	A ~B	1111

 


Figure 51 A | ~B

A - B

F2:0	Function	Result
110	A – B	0010

 


Figure 52 A - B

SLT

F2:0	Function	Result
111	SLT	0000

 


Figure 53 SLT test

Results

Propagation delay

The propagation delay was measured on the worst-case scenario; the worst-case here is the longest path of signals that is the addition part. Thus, the propagation delay of both ALUs' addition was measured.

ALU with carry lookahead adder:

TPLH is 5.82ns and TPHL is 6.3ns as shown below.

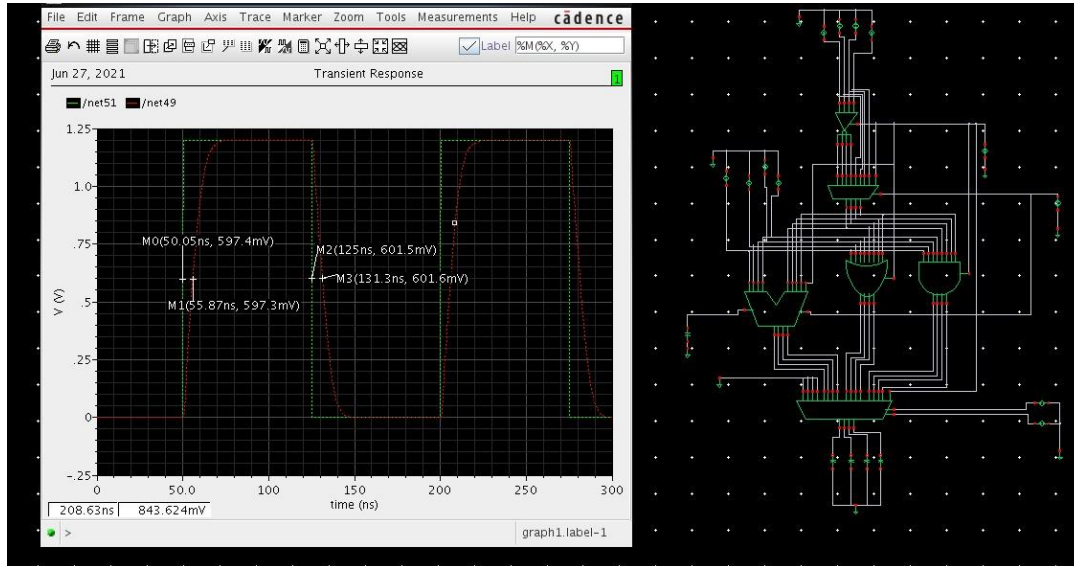


Figure 54 CLA Propagation delay

ALU with ripple adder

TPLH is 5.83ns and TPHL is 6ns as shown below.

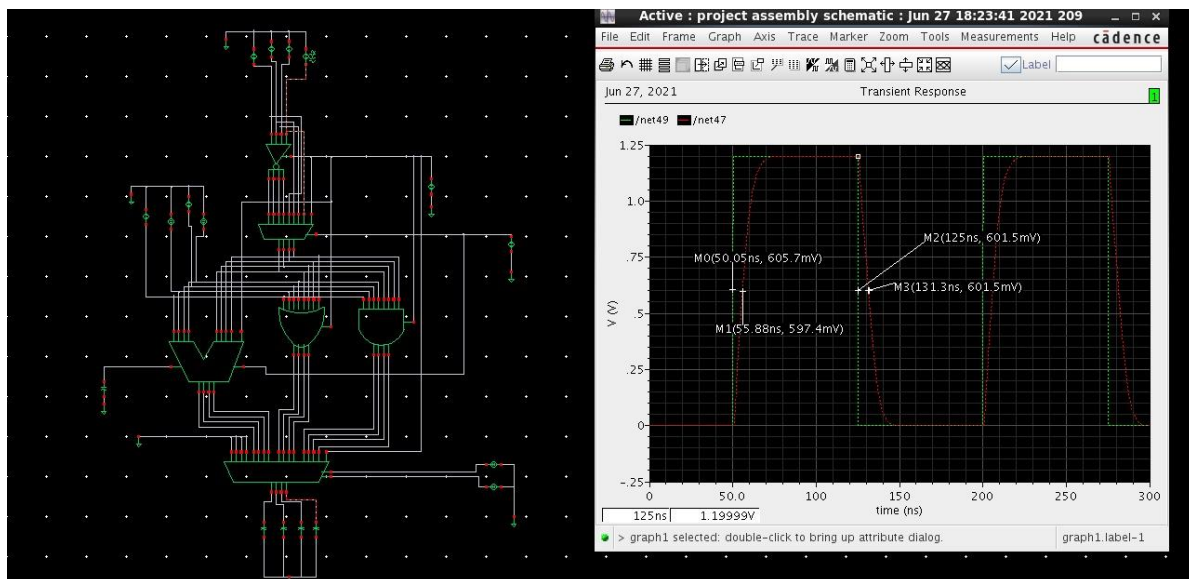


Figure 55 Ripple Adder propagation delay

Maximum power consumption

ALU by carry lookahead adder

The power consumption was measured by the simulation

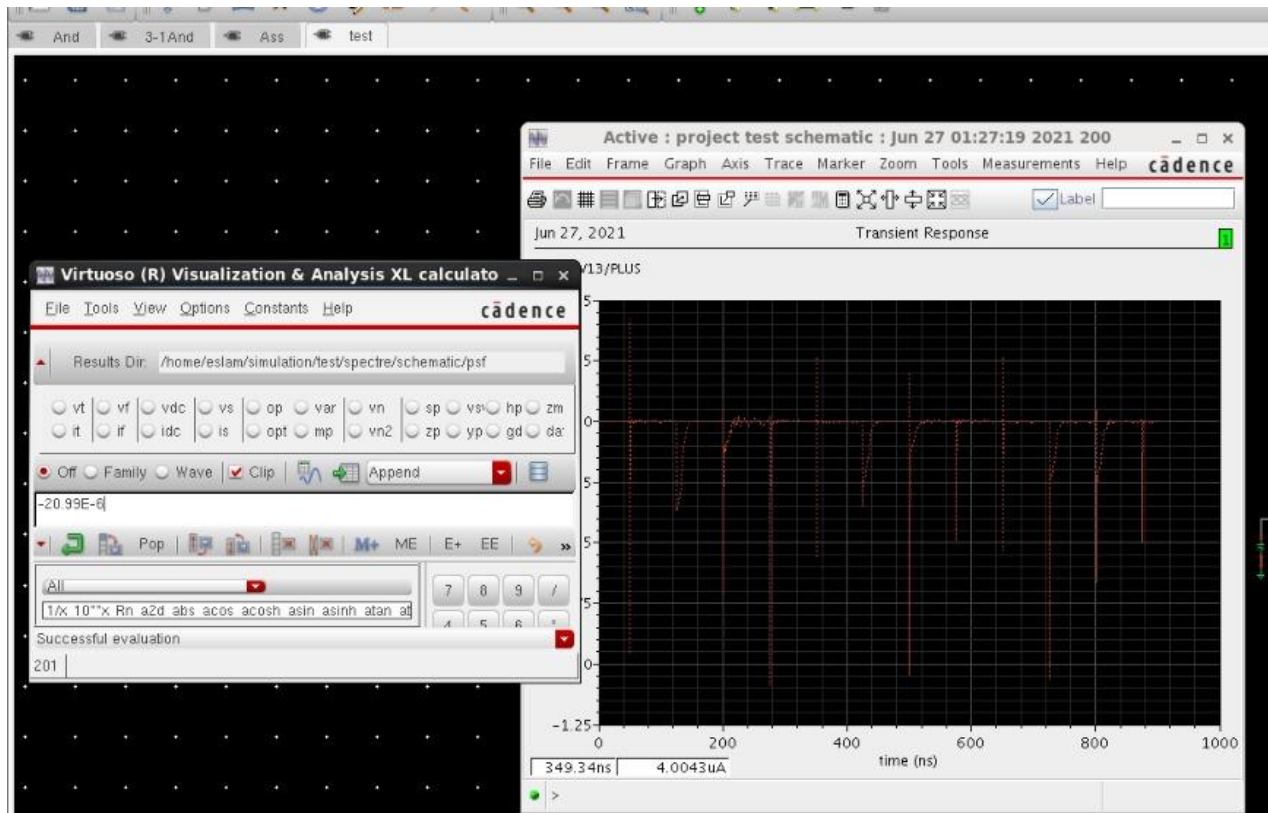


Figure 56 ALU with CLA Power Consumption

ALU by ripple adder

The power consumption was measured by the simulation

 


Figure 57 ALU with ripple adder power consumption

Comparison and conclusion

Aspect of comparison	Carry lookahead ALU	Ripple carry ALU
Number of used transistors	636	568
Power dissipation	20.99 μW	20.64 μW
Propagation delay	TPLH = 5.82ns TPHL = 6.3ns	TPLH = 5.83ns TPHL = 6ns

The number of used transistors could have been larger than the current number (772 in case of CLA and 704 in case of ripple adder) if we used the multiple input one output combinational logic gates with designed logic gates instead of designing them as MOSFETs. The performance of the two adders is nearly the same because we are working on a scale of 4 bits, if the number increases the output will be different. Finally, the number of used transistors in CLA is more than that used with ripple adder, but it is not a big difference.